

VERIFICATION OF BOOLEAN THEOREMS

EXP.NO. : 2

AIM:

To study and verify the Boolean theorems using logic gates.

COMPONENTS REQUIRED:

S.No.	Apparatus	Specifications	Quantity
1.	IC Trainer kit	--	1 no
2.	Logic gate IC's	IC 7404, IC 7408	1no each
3.	Logic gate IC's	IC 7402, IC 7486	1no each
4.	Connecting wires	--	1 set

Theorems:

1. Idempotent laws:

a) $x + x = x$

b) $x \cdot x = x$

2. Identity law:

$x + 1 = x$

3. Null law:

$x \cdot 0 = x$

4. Involution law (or) double negation law:

$(x')' = x$

5. Associative law:

$x + (y + z) = (x + y) + z$

$x \cdot (y \cdot z) = (x \cdot y) \cdot z$

6. Demorgan's law:

$(x + y)' = x' \cdot y'$

$(x \cdot y)' = x' + y'$


7. Adsorption theorem:

$x + (x \cdot y) = x$


$x \cdot (x + y) = x$

1. **Idempotence laws:**

a) $x + x = x$

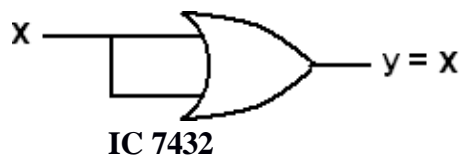

b) $x \cdot x = x$

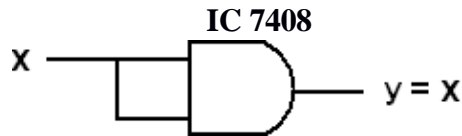


TRUTH TABLE

x	$x + x = x$
0	0
1	1

x	$x \cdot x = x$
0	0

2. **Identity law:**


$x + 1 = 1$

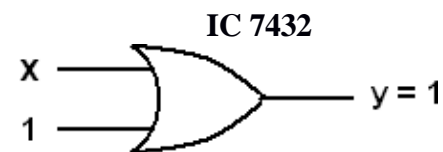

x	$x + 1 =$
0	1
1	1

3. **Null law:**

$x \cdot 0 = 0$

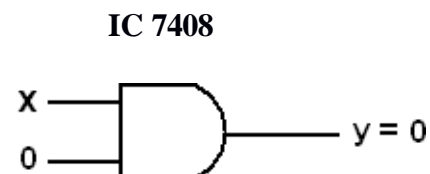


x	$x \cdot 0 = 0$
0	0

4. **Involution law (or) double negation law:**

$(x')' = x$

IC 7404 IC 7404

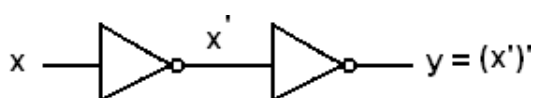


x	x'	$(x')' = x$
0	1	0


5. Associative law:

a) $x + (y + z) = (x + y) + z$

L.H.S

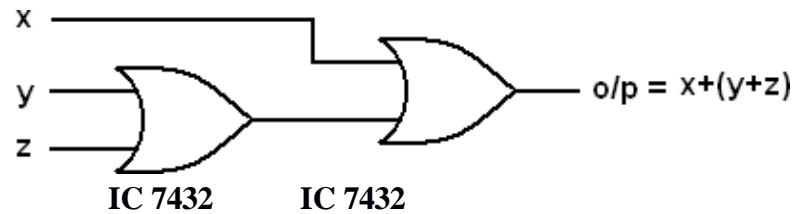


R.H.S

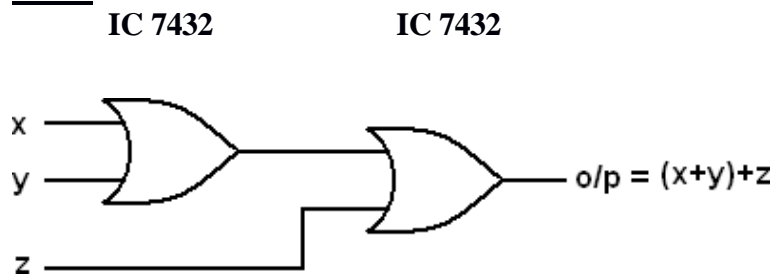


b) $x \cdot (y \cdot z) = (x \cdot y) \cdot z$

L.H.S

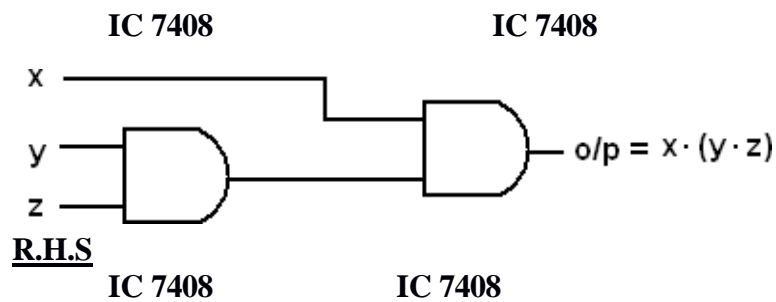

R.H.S

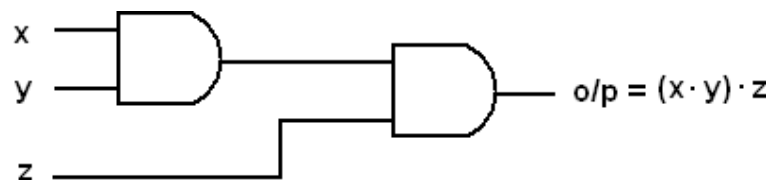

x	y	z	$y + z$	$x + (y + z)$	$x + y$	$(x + y) + z$
0	0	0	0	0	0	0
0	0	1	1	1	0	1
0	1	0	1	1	1	1
0	1	1	1	1	1	1
1	0	0	0	1	1	1
1	0	1	1	1	1	1
1	1	0	1	1	1	1
1	1	1	1	1	1	1

x	y	z	$y \cdot z$	$x \cdot (y \cdot z)$	$x \cdot y$	$(x \cdot y) \cdot z$
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	1	0	0	0
1	0	0	0	0	0	0
1	0	1	0	0	0	0
1	1	0	0	0	1	0
1	1	1	1	1	1	1

6. Demorgan's law:


a) $(x + y)' = x' \cdot y'$

L.H.S


IC 7432

IC 7404

x	Y	x + y	(x + y)'	x'	y'	x' . y'
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0

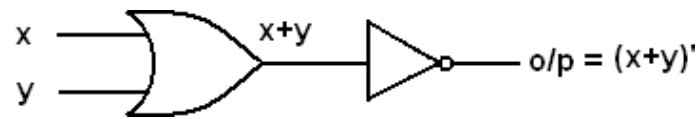


R.H.S

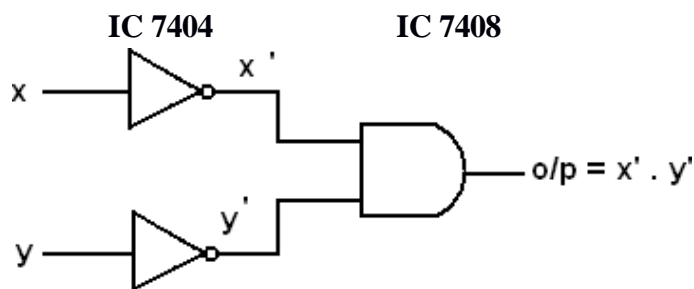


b) $(x \cdot y)' = x' + y'$

L.H.S

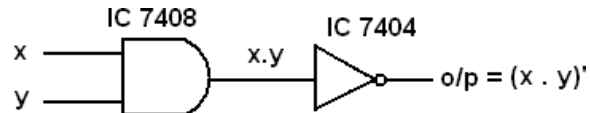

R.H.S


x	Y	x.y	(x.y)'	x'	y'	x'+y'
0	0	0	1	1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0

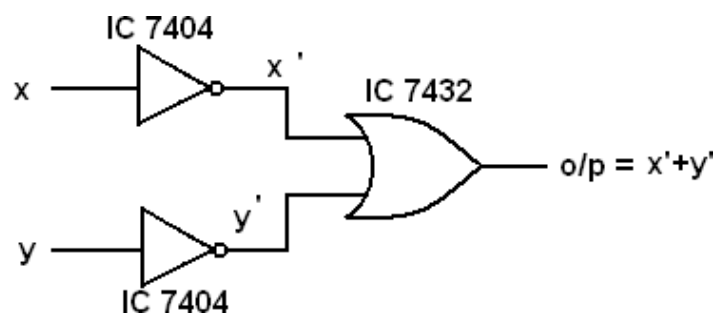


7. Adsorption theorem:

a) $x + (x \cdot y) = x$

x	y	x . y	x + (x . y) = x
0	0	0	0
0	1	0	0
1	0	0	1

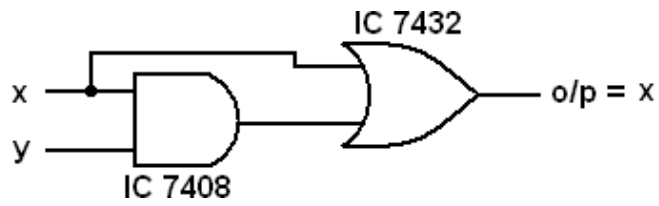

b) $x.(x + y) = x$

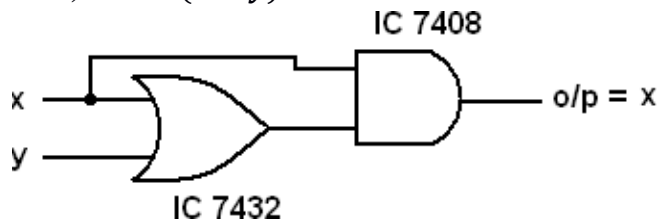

x	y	$x + y$	$x.(x + y)$ $= x$
0	0	0	0
0	1	1	0
1	0	1	1
1	1	1	1

Procedure:

1. Connections are made as per the circuit diagram for each of the theorems.
2. Switch on the IC trainer kit.
3. Apply logic inputs 0 or 1 to input variables
4. Verify the truth table by observing the output indicators for all the theorems.

Result:

Thus, the Boolean theorems and Laws are studied and verified using logic gates.